

**EE212**  
**SPRING 2019-2020 SPRING**  
**HOMEWORK**  
**ALL SECTIONS**

**Assigned: June 10, 2020**

**Due: June 29, 2020**

**To be uploaded to ODTUClass before midnight (23.55)!**

**Late submissions will not be accepted**

**Rules and Reminders**

- Include your name and id number to your circuits by adding text comment.
- Your report should be in order and easy to read. You are expected to upload a single .pdf file.
- If you have troubles with LTSpice software, reinstall the newest version from following url.: <https://www.analog.com/en/design-center/design-tools-and-calculators/ltspice-simulator.html>

Construct the circuit in figure 1 on a circuit simulator software, preferably LTSpice.

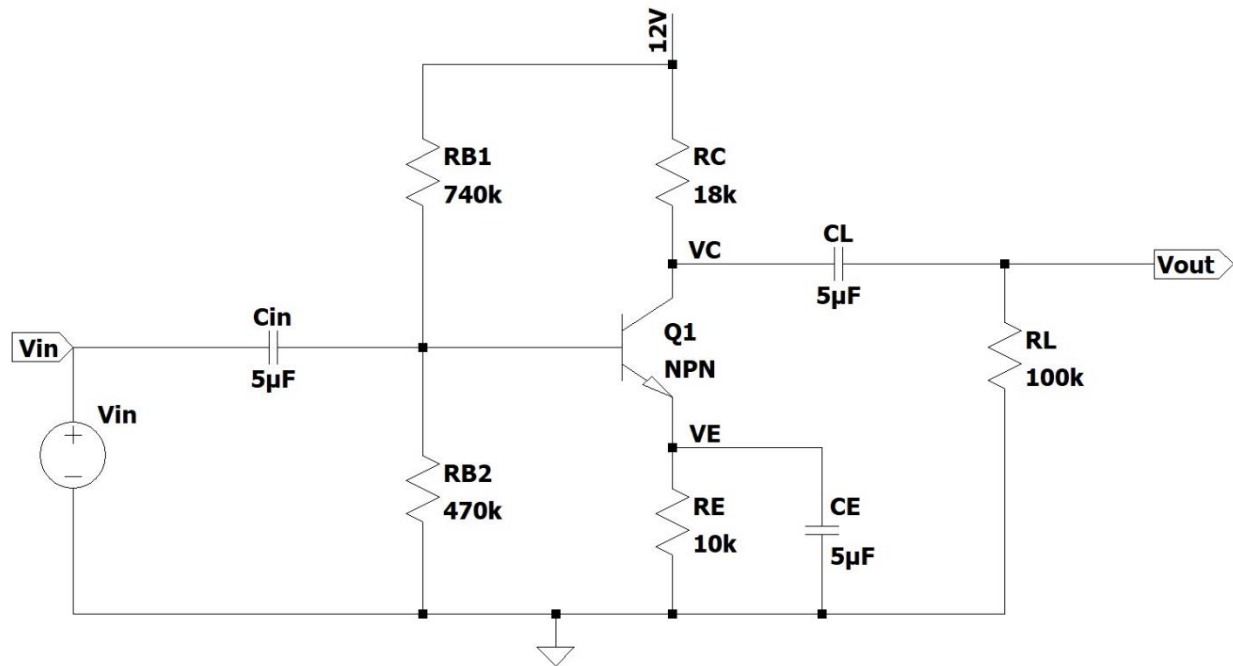


Figure 1. Common-Emitter amplifier

### Part 1)

- i) Edit the default NPN model to change the forward active current gain to ( $\beta_f$ ) 200. Run transient analysis for 0.5 ms and observe the input & output voltages. What is the AC voltage gain of the circuit? Specify how you selected the frequency and amplitude of  $V_{in}$  and find a limit to the amplitude of  $V_{in}$  for a reasonable operation. (Hint: You can observe input and output waveforms for various amplitude of  $V_{in}$ )
- ii) Now you will see how the output voltage changes with the different gain. Run transient analysis for different  $\beta_f$  of 50, 100, 200 and 400. Observe the output voltages for different  $\beta_f$ s. Comment on what you have observed in this part. Is the output gain linearly proportional to the  $\beta_f$ ? Why or why not? Comment on possible reasons.
- iii) Change the collector resistance ( $R_C$ ) to 50 k $\Omega$  (with  $\beta_f = 200$ ). Run the transient simulation. Observe the output voltage and voltage gain. Comment on it.
- iv) Now you will use the last two digits of your ID number, call them XY. Have the software perform transient analysis for load resistance of ( $R_L$ ) of (X+Y+1) k $\Omega$ , XY k $\Omega$ , 50 k $\Omega$ , and (100-XY) k $\Omega$ . Observe the output for four different load resistances. Comment on what you have observed in this part. For instance, ID number of 1234567: X=6, Y=7, (X+Y+1)=14, XY=67, 100-XY=33.

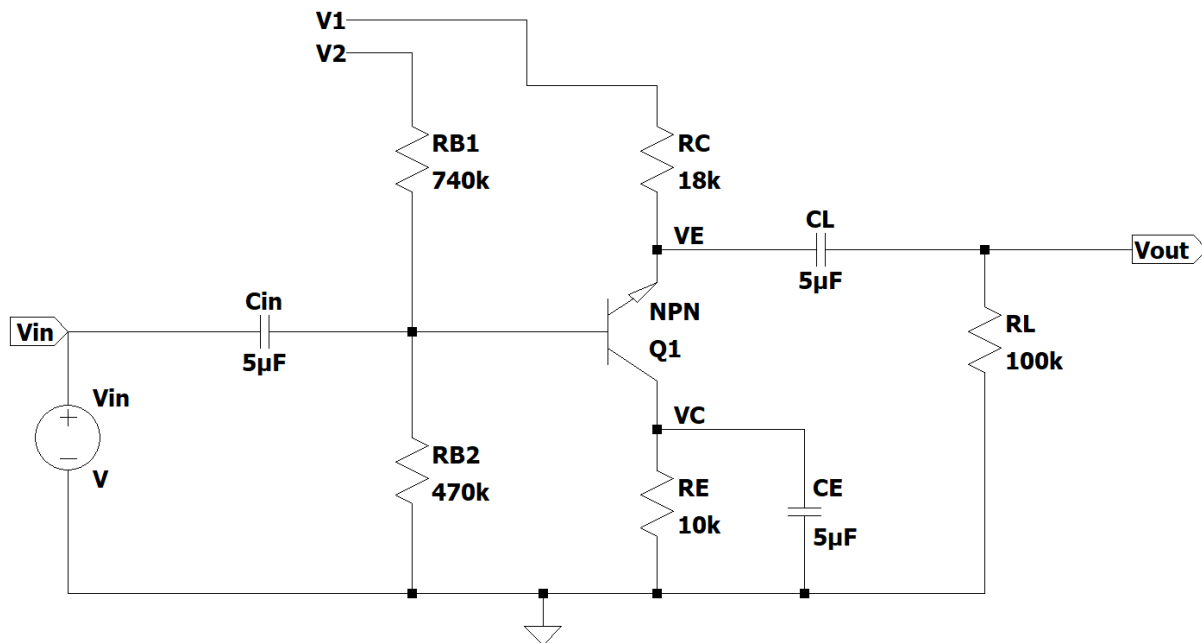


Figure 2. Common-Emitter amplifier (reverse-active mode)

## Part 2)

- i) Now cut the connection between RB1 and RC resistors (figure 1). Connect different voltage sources for both of the open connections. Using 'DC Sweep', sweep the voltage sources accordingly:  
**(V1):** The one connected to RC: Start value = 0 V, Stop value = 12 V, Linear increment = 0.1V.  
**(V2):** The one connected to RB1: Start value = 1 V, Stop value = 7 V, Linear increment = 1 V.  
 Plot the  $I_C$  vs.  $V_{CE}$  diagram. Observe the graph and comment on operation regions of the transistor. ( $\beta_F = 200$ ).
- ii) Construct the circuit in figure 2. Using the same DC sweep parameter at i); Plot the  $I_C$  vs.  $V_{CE}$  diagram. Observe the graph and comment on operation regions of the transistor. What are the differences between these two plots? Comment on your observations.
- iii) Using transient analysis, find reverse active current gain ( $\beta_R$ ) of the transistor.